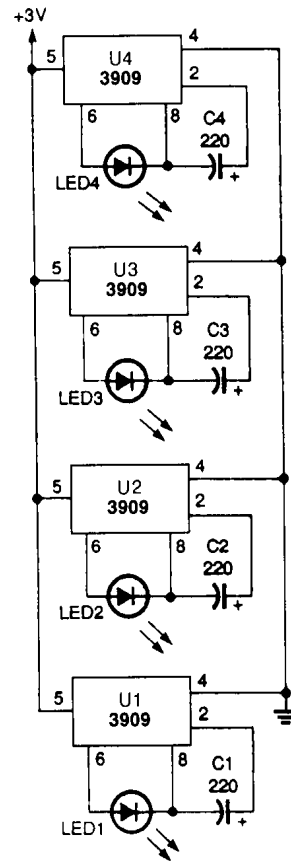


FLASHING CHRISTMAS LED DISPLAY



Using LEDs and 3909 ICs, you can make a flashing-light circuit that will run for months on two AA batteries.