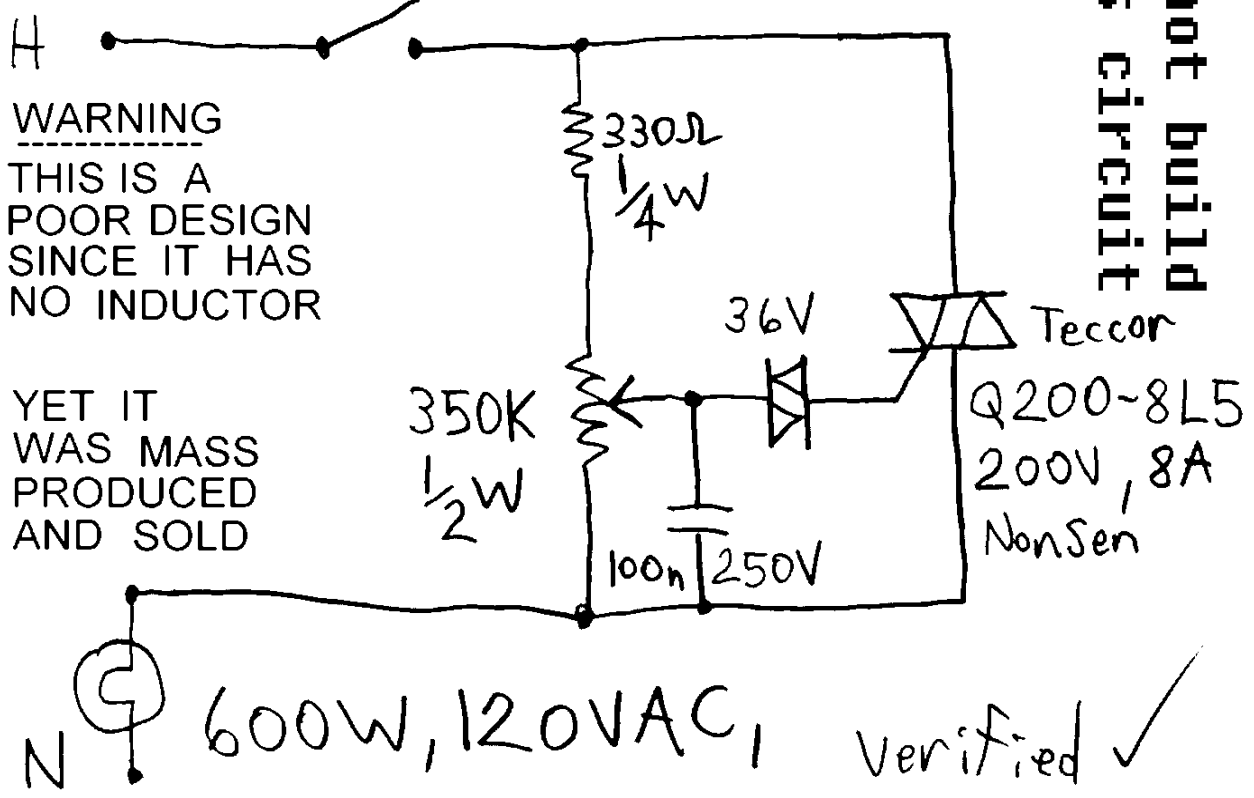


600W 120VAC Lamp Dimmer - Manufacturer did not bother to design in the usual choke.

[HOME](#)

Incadescent Lamp Dimmer

Do not build
this circuit



This must generate an awfull lot of RFI without a choke! The house wiring supplies the di/dt limiting. This is a CHEAP design which exhibits hysteresis at dim settings. Not everything made and sold to the public is top notch.



[HOME](#)

